

EXPERIMENT No.3Computation of Transmission Line Parameters:
ABCD parametersAim


To compute the ABCD parameters of given nominal T and nominal Pi model transmission line.

Software Platform

Scilab

Theory

Nominal T Representation

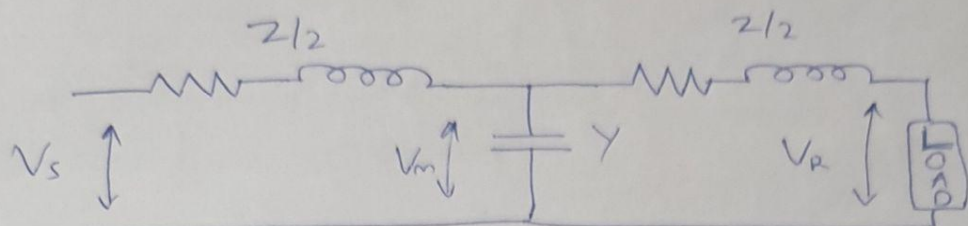

$$\bar{I}_S = Y V_m + \bar{I}_R \quad V_S = \left(\frac{Y}{2} Z + 1 \right) V_R + Z \left[\frac{Y}{4} Z + 1 \right]$$

$$V_m = \frac{2 (V_S + V_R)}{Y Z + 4}$$


$$\bar{I}_S = Y V_R + \left(\frac{Y}{2} Z + 1 \right) \bar{I}_R$$

$$V_S = A V_R + B \bar{I}_R$$

$$\bar{I}_S = C V_R + D \bar{I}_R$$

$$A = \frac{Y Z}{2} + 1, \quad B = Z \left(\frac{Y Z}{4} + 1 \right), \quad C = Y, \quad D = \left(\frac{Y Z}{2} + 1 \right)$$

Nominal π Network

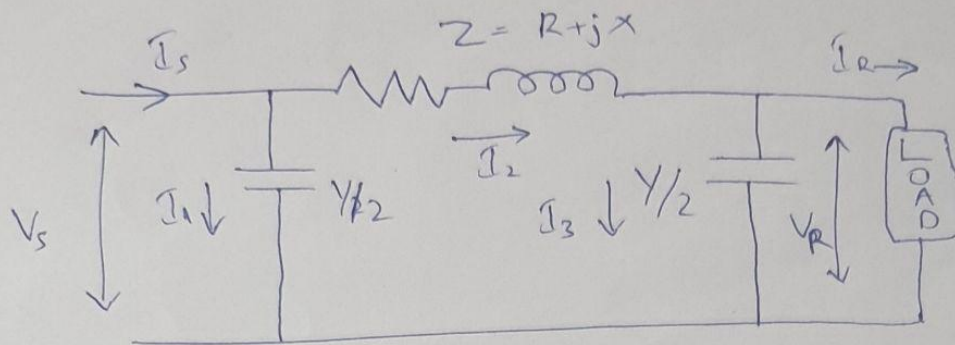

$$I_s = I_1 + I_2 \quad I_2 = I_3 + I_R \quad V_s = AV_R + BI_R$$

$$I_s = CV_R + DI_R$$

$$I_s = \frac{Y}{2} V_s + \frac{Y}{2} V_R + I_R$$

$$V_s = V_R + Z I_2$$

$$V_s = \left(\frac{ZY}{2} + 1 \right) V_R + Z I_R$$

$$I_s = Y \left(\frac{YZ}{4} + 1 \right) V_R + \left(\frac{YZ}{2} + 1 \right) I_R$$

$$A = \frac{YZ}{2} + 1 \quad B = Z \quad C = Y \left(\frac{YZ}{4} + 1 \right) \quad D = \left(\frac{YZ}{2} + 1 \right)$$

Program

Problem 1

A balanced 3-phase load of 30 MW is supplied at 132 KV, 50 Hz and 0.85 pf lagging by needs of a transmission line. The series impedance of a single conductor is $(20+j52)$ ohms and the total phase neutral admittance is 315×10^{-6} Siemen. Using nominal T method determine Transmission line ABCD-parameters and the regulation of the line.

Problem 2

A 3 phase, 50 Hz, 100 Km line has a resistance, inductive reactance and capacitive shunt admittance of $0.1\Omega/\text{Km}$, $0.2\Omega/\text{Km}$ and $4 \times 10^{-6} \text{ S/Km}$ per phase. If the line delivers 10 MW at 110 KV and 0.8 pf lagging, determine the transmission line ABCD-parameters and the regulation of the line using nominal-pi method.

Sample Program (All)

```
1. clc;
2. clear;

3. model=input("Enter 0 for T model and 1 for Pi model:")
4. rkm=input("Enter series resistance per km:")
5. lkm=input("Enter series reactance per km(with %i):")
6. ykm=input("Enter shunt admittance per km(with %i):")
7. distance=input("Enter the length in km:")

8. r=distance*rkm
9. l=distance*lkm
10. y=distance*ykm

11. z=r+l
12. temp=z*y/2
13. a=temp+1
14. d=a

15. if model==0 then
16. b=z*(1+(temp/2))
17. c=y
18. elseif model==1 then
19. c=y*(1+(temp/2))
20. b=z
21. end

22. disp('The values of ABCD parameters are ')
23. disp('A = ',a)
24. disp('B = ',b)
25. disp('C = ',c)
26. disp('D = ',d)
```

Sample Output – 1

```
Enter 0 for T model and 1 for Pi model:0
Enter series resistance per km:20
Enter series reactance per km(with *%i):52*%i
Enter shunt admittance per km(with *%i):315*10^-6*%i
Enter the length in km:1

"The values of ABCD parameters are "
"A = " 0.99181 + 0.00315i
"B = " 19.8362 + 51.81856i
"C = " 0. + 0.000315i
"D = " 0.99181 + 0.00315i
```

Sample Output – 2

```
Enter 0 for T model and 1 for Pi model:1
Enter series resistance per km:0.1
Enter series reactance per km(with *%i):0.2*%i
Enter shunt admittance per km(with *%i):4*10^-6*%i
Enter the length in km:100

"The values of ABCD parameters are "
"A = " 0.996 + 0.002i
"B = " 10. + 20.i
"C = " -0.0000004 + 0.0003992i
"D = " 0.996 + 0.002i
```

Result

ABCD parameters of given nominal T and nominal Pi model transmission lines were calculated using Scilab and verified.